

CSE350

Digital Electronics and Pulse Techniques


# Lab Report

Name: Eftykhar Rahman

ID: 18301041

Section: CSE5

Submission Date: 10/7/21

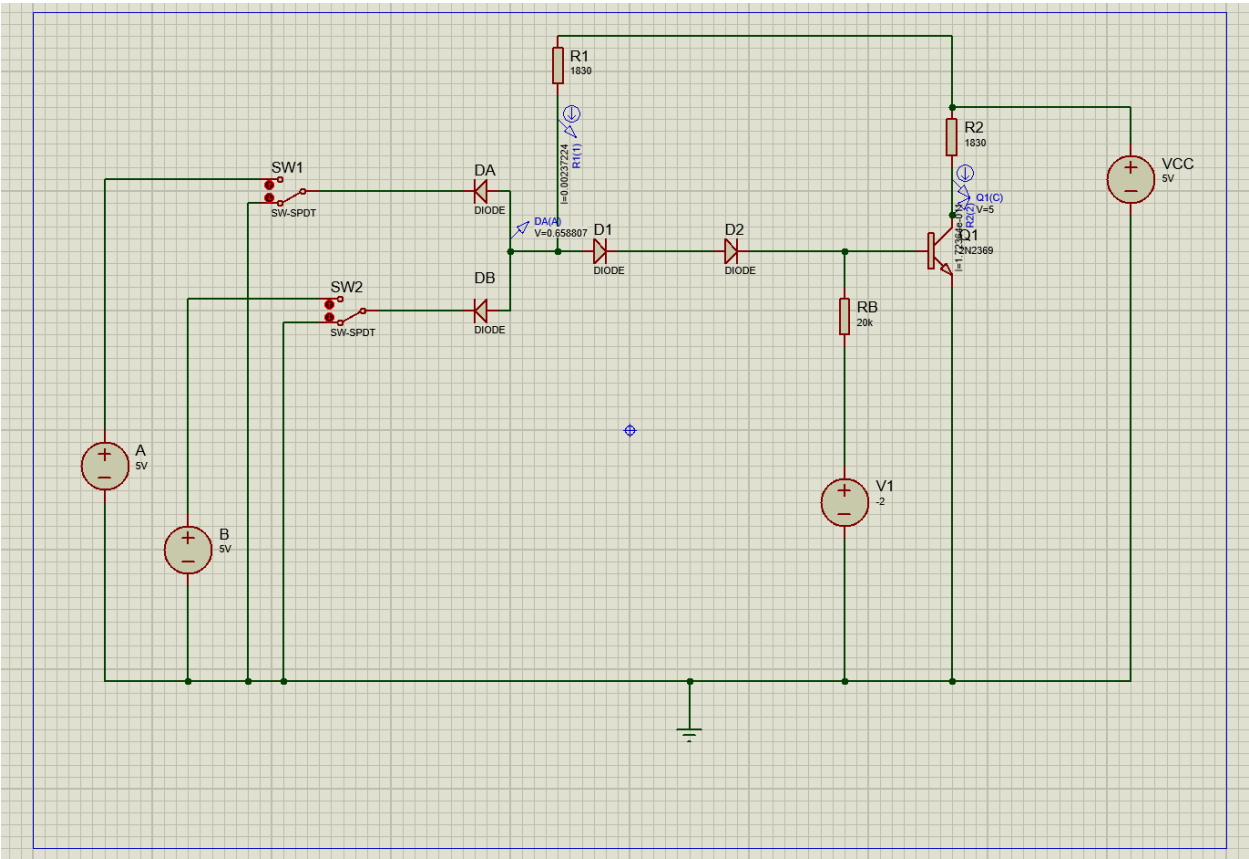

Input A	Input B	$V_{DA}$	$V_{DB}$	$V_P$	$I_{R1}$	$I_{R2}$	$V_b$	Output Y
0	0	0.658	0.658	0.658	0.00237	$2.2 \times 10^{-4}$	-0.5162	5
0	1	0.676	-4.434	0.676	0.00236	$2.2 \times 10^{-4}$	-0.4999	5
1	0	-4.434	0.676	0.676	0.00236	$2.2 \times 10^{-4}$	-0.4999	5
1	1	-2.762	-2.762	2.156	0.00155	0.00267	0.8235	0.0991

Input A	Input B	$V_P$	$V_b$	Output Y
1	0	0.676	-0.499	5
1	1	2.156	0.8235	0.0991


18301091

**Aclobet-N<sup>TM</sup>**

Answer to the question  
Number - 1

18301041

Input  $A = 5V$  ,  $B = 5V$

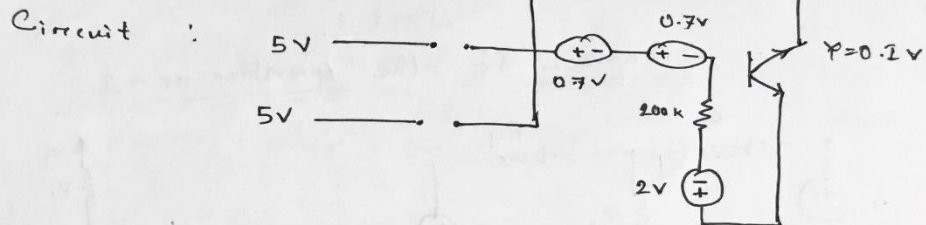

Answer to the question  
Number - 2

Input A	Input B	Output Y
1	0	5
1	1	0.1

Input 1 is connected to +5V as constant and another value is variable means changed / changeable.

By keeping input  $A = 5V$  constant and changing Input B to 0 and 1 the circuit act as Inverter or Not gate.

Answer to the question  
number - 3

14301041

Considering  $A = 0V$ ,  $B = 5V$  diode  $D_B$  is off and diode  $D_A$  is on.  $V_p \approx 0.7$  As a result transistor is cut off and  $V = 5V$ .

Again, when the input  $A = 5V$ ,  $B = 0V$  the diode is in forward bias and ON. So, diode  $D_A$  is in Reverse bias and OFF. So,  $V_p = 0.7$  and transistor will be cut off and  $V = 5V$ .

Answer to the question  
number - 04

Input  $A = 5V$ ,  $B = 0V$  then  $V_p = 0.7V$  and  $V_p$  should be minimum  $2.1V$  and turned ON.

$V_p = 0.7$  and  $V_b = -0.49V$  that means the bias voltage of transistor is  $-0.49V$  which is less than  $0.5V$ . that is why it is turned ON.

$V_D = -0.499V < 0.5V$  thus transistor will be in cutoff mode.



Answer to the question no-5

Input A	Input B	output Y
0V	0V	5V
0V	1V	5V
1V	0V	5V